

Professor: J.D. Wilson Time available: 80 mins Value: 20%

Instructions: *Closed book exam. Please record your answers in the exam booklet. Pertinent data and diagrams are at the back, and should be read before answering any questions.*

Multi-choice (20 x $\frac{1}{2}\%$ \rightarrow 10%)

1. In the context of the simplest environmental instruments we have to do with “d.c. circuits” (slowly varying signals). To be sure of the absence of “noise” in such a circuit, one should inspect the signal with a/n _____


- (a) multimeter
- (b) oscilloscope ✓✓
- (c) chart recorder
- (d) data-logger
- (e) grounded receiver

2. To connect an oscilloscope (lo = power-line ground) to display a potential difference between two points in a d.c. circuit, which of the steps below would be wrong?

- (a) ascertain that the normal performance of the circuit will not be disrupted by pulling one of the two circuit points to p.l.g.
- (b) adjust the zero on the scope
- (c) adjust the full-scale-range on the scope to a suitable value for the expected measurement
- (d) adjust the scope triggering to “auto”
- (e) select a.c. coupling ✓✓

3. If $V_o = 2\text{ V}$, $R_1 = 10\text{ K}\Omega$ and $R_2 = 5\text{ K}\Omega$, then the supply voltage V is _____ volts

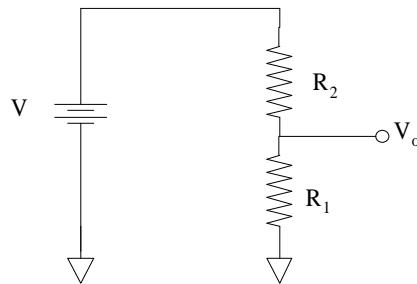- (a) 5
- (b) 3 ✓✓
- (c) 2
- (d) 1.33
- (e) 0.66



4. You are given two points on the resistance-temperature curve of a thermistor: (10 C, 75 K Ω) and (20 C, 50 K Ω). Between these points your best guess for the “slope” dR/dT of the resistance-temperature curve is _____
- (a) 25 K Ω C $^{-1}$
 - (b) -25 K Ω C $^{-1}$
 - (c) 2.5 K Ω C $^{-1}$
 - (d) -2.5 K Ω C $^{-1}$ ✓✓
 - (e) zero
5. If the resistance measured between a voltage-receiver ground and its inputs is large and equal for *both* inputs (‘hi’ and ‘lo’, also sometimes labelled V^+ , V^-), then the receiver is called _____
- (a) hi gain
 - (b) differential ✓✓
 - (c) single-ended
 - (d) grounded
 - (e) floating
6. Suppose a data-logger displays a number N representing the voltage ($V^+ - V^-$) across its two input terminals, and that it can be assumed that the logger is “linear,” ie., that $N = \alpha(V^+ - V^-) + \beta$. Furthermore, suppose the Full Scale Range (FSR) of the logger is ± 10 volts. If we measure a reading N_1 when ($V^+ - V^-$) = 10.0 volts, and a reading N_2 when ($V^+ - V^-$) = -10.0 volts, then the quantity $(N_1 - N_2)/20.0$ is _____
- (a) the “offset” of the logger, β
 - (b) zero
 - (c) variable
 - (d) the sensitivity, α ✓✓
 - (e) none of the above
7. Following on from the above question, the purpose of short-circuiting the input to a data-logger and noting the indicated measurement (N_0) is:
- (a) To remove any common mode voltage
 - (b) To assess the necessary full scale range setting
 - (c) To ground the input
 - (d) To float the input
 - (e) To ascertain the “zero reading” or “offset” β ✓✓

8. Generalizing from the case shown, it can be concluded that the charge-voltage ($V - q$) characteristic of a battery is

- (a) that of a capacitor
- (b) that of a resistor
- (c) unlike that of a capacitor ✓✓
- (d) Ohm's Law
- (e) none of the above

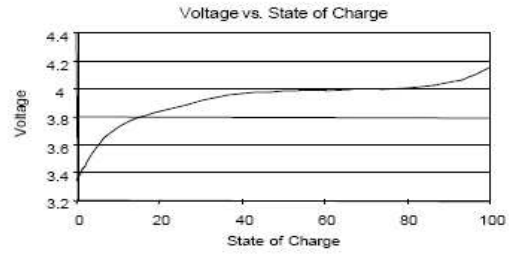


Figure 5. Open Cell Voltage of Lithium Polymer Battery

9. Suppose the fastest fluctuations of a certain signal $x = x(t)$ were characterized by a frequency f_{max} (or equivalently a period $T_{min} = 1/f_{max}$). For an instrument to faithfully measure this signal, its time constant τ (characterizing its step response) would need to satisfy _____


- (a) $\tau \gg T_{min}$
- (b) $\tau \ll T_{min}$ ✓✓
- (c) $\tau = T_{min}$
- (d) $1/\tau = f_{max}$
- (e) $\tau^2 + 2\tau - 1 = 0$

10. A shaft is rotating 30 times per minute. Its angular frequency in [radians sec^{-1}] is:

- (a) 0.5
- (b) 180
- (c) π ✓✓
- (d) 2π
- (e) 360

11. Given two identical thermistors R_{1T}, R_{2T} and two identical control resistors R_{1c}, R_{2c} , a differential temperature sensor could be constructed by placing _____ in the full bridge shown

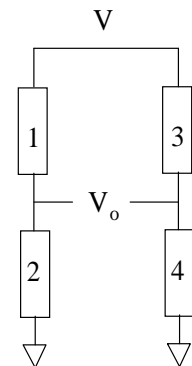- (a) one thermistor in each of slots 1,2
- (b) one thermistor in each of slots 3,4
- (c) one thermistor in each of slots 1,3
- (d) one thermistor in each of slots 2,4
- (e) both (c) and (d) would work ✓✓



12. The internal resistance of a particular $V_s = 12$ volt battery is 1Ω . If this battery is connected across an 11Ω load, the power dissipated in the load is _____ Watts

- (a) $1/11$
- (b) $11/12$
- (c) 1
- (d) 11 ✓✓
- (e) 12

13. Suppose a symmetric square wave with period T and levels $\pm A$ volts is input to an RC lowpass filter whose time constant $\tau = T$. The voltage V_o across the capacitor (ie. output voltage) will be _____


- (a) completely steady at $V_o = 0$
- (b) a square wave of span $\pm A_o$, with $A_o > A$
- (c) a square wave of span $\pm A_o$, with $A_o = A$
- (d) a square wave of span $\pm A_o$, with $A_o < A$
- (e) a wave centred on $V_o = 0$, of span $\pm A_o$ with $A_o < A$, that lacks the sharp transitions (edges, or ‘step changes’) of the input wave ✓✓

14. A tank of volume D^3 is kept in a well-stirred condition by a powerful fan, and initially contains a pure gas “A.” At $t = 0$ it begins to be flushed by an inflow (volumetric flow rate Q [$\text{m}^3 \text{s}^{-1}$]) of pure gas “B,” that displaces (at equal rate) mixed gas through an outlet. The transition of the tank’s contents from “pure A” to “pure B” takes place with time constant

- (a) $(A - B)/Q$
- (b) $A - B$
- (c) D^3/Q ✓✓
- (d) Q/D^3
- (e) $A - BD^3/Q$


15. If $T_1 = T_2$ then this arrangement measures _____ with a sensitivity determined by metals _____

- (a) $|T_1 - T_3|$; (A,B)
- (b) $|T_1 - T_3|$; (B,C)
- (c) $|T_1 - T_3|$; (A,C) ✓✓
- (d) $|T_2 - T_3|$; (A,B)
- (e) C; (A,B)

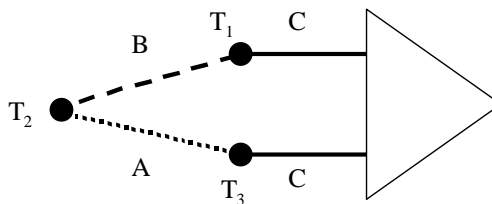


16. A thermistor with characteristic $R(T) = R(T_0) \exp \left[\beta \left(\frac{1}{T} - \frac{1}{T_0} \right) \right]$ is placed as R_2 in the circuit shown, with $R_1 = R(T_0)$. If $T > T_0$ then _____ and _____

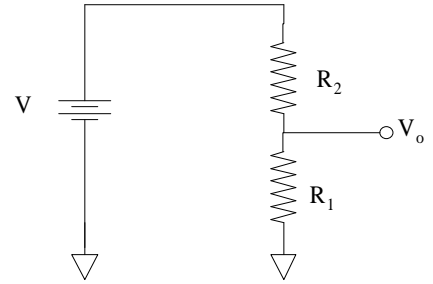- (a) $R > R(T_0)$; $V_o > V/2$
 (b) $R < R(T_0)$; $V_o > V/2$ ✓✓
 (c) $R > R(T_0)$; $V_o < V/2$
 (d) $R < R(T_0)$; $V_o < V/2$



17. If the circuit shown is intended to solve the differential equation $\alpha \frac{dy}{dt} = \beta$ (where α, β are constants, and t is time) then the source should be a _____. **The circuit element should have been a capacitor! Question not scored.**

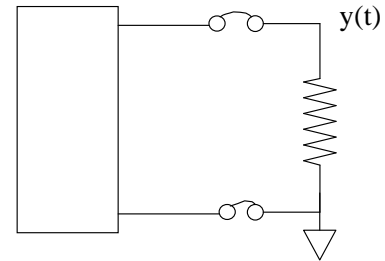- (a) constant current source
 (b) constant voltage source
 (c) alternating current source
 (d) alternating voltage source
 (e) current impulse source



18. A linear temperature sensor has sensitivity α [volts K^{-1}] and is input to a voltage receiver having resolution δV [volts]. The resulting temperature resolution (δT) is

- (a) α
 (b) $\alpha/\delta V$
 (c) $\delta V/\alpha$ ✓✓
 (d) $1/\delta T$
 (e) $\alpha\delta V$

19. If a signal $x = (1, -1, 1, -2, 6)$ then the signal *fluctuation* $x' = x - \bar{x}$ is which series?

- (a) 1, -1, 1, -2, 6
 (b) 0, 2, 0, 3, -5
 (c) 0, 2, 0, -3, 5
 (d) 0, 0, 0, 0, 0
 (e) 0, -2, 0, -3, 5 ✓✓

20. At steady state and neglecting internal heating and any radiation error, it can be said of the energy balance of a dry thermometer $C \Delta T / \Delta t = A(Q^* + Q_H + Q_E) + P$ that
- the dominant term is Q_H
 - every term reduces to zero ✓✓
 - the equation reduces to a balance between $\Delta T / \Delta t$ and Q_H
 - the equation reduces to a balance between P and Q_H
 - the equation reduces to a balance between Q^* and Q_H

Short Answer (10 %)

Answer **two** questions from this section. Give diagrams where appropriate. Justify any assumptions or simplifications you make.

- A thermopile for measuring soil heat flux has been constructed from 20 copper-constantin thermocouples (Seebeck coefficient $40 \mu\text{V C}^{-1}$) connected in series. All the hot junctions are together at a depth $z = 0.01$ m in the soil, while the cold junctions are at depth $z = 0.05$ m. Calculate the magnitude of the thermopile output voltage, if the soil heat flux density is $Q_G = 20 \text{ W m}^{-2}$. (Note: you will need to use Fourier's law of heat conduction

$$Q_G = -\kappa \frac{dT}{dz}$$

where κ is the soil conductivity; assume $\kappa = 1.0 \text{ W m}^{-1} \text{ K}^{-1}$).

Answer:

$|\Delta T| = 0.8 \text{ C}$, so magnitude of the output voltage is $|V| = 20 \times 40 \times 0.8 \mu\text{V} = 0.64 \text{ mV}$ (Note: the 'magnitude' of a number is *by definition* its absolute value.)

- Explain, in terms that should be unambiguous to an intelligent person familiar with the functions of a multimeter, how s/he should proceed in order to determine whether a particular voltage source, having two output terminals labelled (hi, lo), is a floating or a grounded source.

Answer:

- find a convenient conductor whose electrical potential is the same as that of the ground, ie. a point from which there is a low resistance path to ground: for example, the U-ground of an ordinary outlet, or (usually) the steel plumbing
- set the multimeter on its resistance-measuring range, with a full scale setting of $1\text{K}\Omega$ or more ($10\text{K}\Omega$ and $100\text{K}\Omega$ acceptable)
- make sure the multimeter is functioning by checking that it reads 'zero' when the probes are touched together
- measure the resistance from the 'lo' to the identified ground point
- if this is not infinity, the source is not a floating source

- conversely, the measured resistance need not be exactly zero even if your source is grounded... the multimeter will see the resistance down the power cable of the device, for example. Thus a measured resistance of up to about 10Ω is compatible with the source being a grounded source

3. Calculate the bulk heat capacity C [J K^{-1}] of a sphere of copper of radius $r = 0.01$ m, given that copper has density $\rho_c = 2700 \text{ kg m}^{-3}$ and specific heat capacity $c = 900 \text{ J kg}^{-1} \text{ K}^{-1}$. If the total heat flux density to the sphere is $Q = 100 \text{ W m}^{-2}$, calculate the rate of change of the temperature of the sphere.

Answer:

$$C = \frac{4}{3}\pi r^3 \rho_c c = 10.18 \text{ J K}^{-1}.$$

$$\frac{dT}{dt} = \frac{Q 4\pi r^2}{C} = 1.23 \times 10^{-2} \text{ K s}^{-1}$$

Data:

- $C \frac{dT}{dt} = A (Q^* + Q_H + Q_E) + P$

Energy balance for a thermometer having bulk heat capacity C and surface area A . The Q 's are (left-to-right) the net radiative, sensible, and latent heat flux densities (W m^{-2}), and P is (any) internal heating.

- $V_o = V \frac{R_1}{R_1+R_2}$

Output of voltage divider

