


Professor: J.D. Wilson      Time available: 80 mins      Value: 15%

**Instructions:** *Closed book exam. Please record your answers in the exam booklet. Pertinent data are given on back page, and should be scanned before answering any questions.*

**Multi-choice** (10 x  $\frac{1}{2}\%$   $\rightarrow$  5%)

1. In the circuit shown, in which the capacitor and resistor constitute a high-pass RC filter, the battery voltage  $V_s$  is constant. The steady-state output voltage  $V_o$  relative to the floating ground is<sup>1</sup>

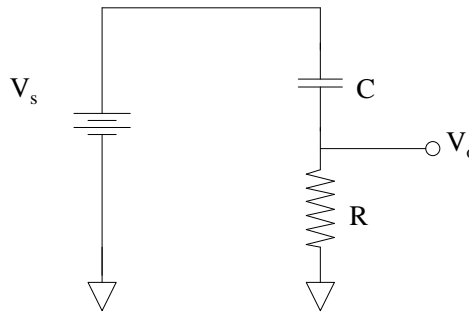- (a) infinite
- (b) fluctuating
- (c)  $V_s$
- (d) zero ✓✓
- (e) none of the above



2. If the battery is replaced by an alternating voltage source  $V_s(t)$  generating a sine wave having frequency  $f$ , then if  $f$  is infinitely-large, the output voltage  $V_o(t)$  relative to the floating ground is<sup>2</sup>

- (a) infinite
- (b) steady
- (c)  $V_s(t)$  ✓✓
- (d) zero
- (e) none of the above

3. If the capacitor in the above circuit is replaced by a resistor identical to the other ( $R$ ), then (irrespective of whether the supply voltage is steady or oscillating)  $V_o/V_s$  is


- (a) 0
- (b)  $1/2$  ✓✓
- (c) 1
- (d) undefined
- (e) none of the above

<sup>1</sup>Hint: a capacitor offers infinite resistance to a steady current.

<sup>2</sup>Hint: a capacitor offers zero resistance to rapidly alternating current.

4. This Wheatstone Bridge is balanced if

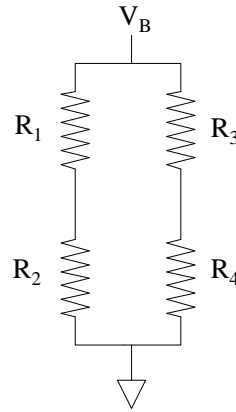- (a)  $R_1 R_2 = R_3 R_4$
- (b)  $R_1 R_3 = R_2 R_4$
- (c)  $R_1 R_4 = R_2 R_3$  ✓✓
- (d)  $V_B = 0$
- (e) all of the above



5. The equation  $Q_{Hx} = -k \frac{dT}{dx}$ , where  $dT/dx$  is a temperature gradient, expresses

- (a) Newton's law of viscosity
- (b) Fourier's law of conduction ✓✓
- (c) Fick's law of diffusion
- (d) all of the above
- (e) none of the above

6. If a thermocouple having Seebeck coefficient  $N = 60 [\mu\text{V K}^{-1}]$  is read by a voltage receiver having offset (ie. zero-error)  $V_{os} = 30 \mu\text{V}$ , the magnitude of the error induced in each reading of temperature difference is \_\_\_\_\_ [K]

- (a)  $\frac{1}{2}$  ✓✓
- (b) 1
- (c) 2
- (d) 30
- (e) 60

7. A certain resistance thermometer has a linear  $R - T$  characteristic, ie. its resistance  $R = R(T)$  varies linearly with temperature according to the equation

$$R = R(T_0) [1 + \alpha (T - T_0)]$$

If this device is placed in a half-bridge, the voltage-temperature characteristic  $V_o(T)$  will be

- (a) the same as that of an RC-lowpass filter
- (b) very sensitive
- (c) offset by an amount  $T_0$
- (d) linear
- (e) non-linear ✓✓

8. If an a.c. voltage has amplitude  $A$ , the mean-square voltage is  $A^2/2$ . Given that the familiar “110 volts” designation for mains power actually cites the “root-mean-square” (r.m.s.) voltage, the voltage *amplitude* at an ordinary mains power outlet must be \_\_\_\_\_ [volts].
- (a) 440
  - (b) 220
  - (c) 110
  - (d)  $110/\sqrt{2}$
  - (e)  $110\sqrt{2}$  ✓✓
9. Regarding an ordinary 3-pin power outlet, \_\_\_\_\_ pins are connected to earth-ground (power-line ground) while \_\_\_\_\_ pins are “hot” (110 volts r.m.s.) relative to power-line ground.
- (a) 1; 2
  - (b) 1; 1
  - (c) 3; 1
  - (d) 2; 2
  - (e) 2; 1 ✓✓
10. The purpose of short-circuiting the input to a digital voltmeter or data-logger, and noting the indicated measurement (N), is to \_\_\_\_\_
- (a) remove any common mode voltage
  - (b) assess the necessary full scale range setting
  - (c) ground the input
  - (d) float the input
  - (e) ascertain the “zero reading” for subsequent corrections ✓✓

## Short Answer/Calculation (5 %)

Answer **one** question from this section. Give diagrams where appropriate to clarify your working, which should be shown. Justify any assumptions or simplifications you make.

1. Suppose a dry aspen leaf (represented as a thin disc of diameter  $d = 0.05$  m) is measured to be  $0.2^\circ\text{C}$  warmer than the wind, which is blowing over the leaf at speed  $U = 1$  m s<sup>-1</sup>. Calculate the net radiative heat load on the leaf,  $Q^*$ . Assume the air has density  $\rho = 1$  kg m<sup>-3</sup>; for other details see data at end of paper.

**or**

2. Draw a tidy and complete circuit schematic representing a half-bridge (resistors  $R_1, R_2$ ) that is driven by a floating voltage source (internal resistance  $R_s$ ), and whose output voltage  $V_o$  (voltage relative to ground measured at the node between  $R_1, R_2$ ) is monitored by a single-ended voltage receiver (input resistance  $R_{in}$ ).

## Long Answer (5 %)

Write up to two pages, including diagrams, on **one** of the topics given. Please give a well-constructed and interesting response, in good English (good organization, good spelling, good grammar), using essay- or point-by-point style, and based around a small number of key points.

1. Suppose you are given a function generator capable of producing a sine wave of fixed amplitude  $A_s$  and (any) arbitrary frequency  $f$ . You are also given an oscilloscope, a resistor of known resistance  $R$ , and a capacitor of *unknown* capacitance  $C$ . Using appropriate diagrams and explanations, describe how, using the given supplies, you might determine the value of  $C$ . (Hint: use the properties of the RC lowpass filter, concerning which some data are given at the back of the exam).

**or**

2. Write an essay explaining in what sense there is “commonality” in the behaviors of a lowpass RC filter, and an ordinary thermometer (in other words, explore the parallels between these systems). This is probably easiest done by focusing on the *step response* (see relevant data at back of exam).

## Data:

- Kinematic viscosity of air:  $\nu \approx 1.5 \times 10^{-5} [m^2 s^{-1}]$
- Thermal diffusivity<sup>3</sup> of air:  $\kappa \equiv D_H \approx 2.1 \times 10^{-5} [m^2 s^{-1}]$
- Specific heat capacity of air at constant pressure:  $c_p \approx 1000 [J kg^{-1} K^{-1}]$
- $C \frac{dT}{dt} = A ( Q^* + Q_H + Q_E ) + P$

Energy balance for a thermometer having bulk heat capacity  $C$  and surface area  $A$ . The  $Q$ 's are (left-to-right) the net radiative, sensible, and latent heat flux densities ( $W m^{-2}$ ), and  $P$  is (any) internal heating.

- $\frac{dV_o}{dt} = \frac{V_s(t) - V_o}{\tau}$

Differential equation giving the relationship between the output  $V_o(t)$  from a lowpass RC filter (time constant  $\tau = RC$ ) and the input  $V_s(t)$ . The particular case of the “step response” corresponds to the specification: at  $t = 0$ ,  $V_o = V_s = 0$ , while for  $t > 0$ ,  $V_s = \text{constant}$ .

- $y(t) = Y_2 + (Y_1 - Y_2) \exp\left(-\frac{t}{\tau}\right)$

Response of a 1<sup>st</sup> order (RC lowpass type) system to step  $Y_1 \rightarrow Y_2$  in input.

- $Q_H = \rho c_p \frac{T_1 - T_2}{r_H}$

Ohm's law model for sensible heat exchange.

- $r_H = \frac{d}{D_H N_u} [s m^{-1}]$

Resistance  $r_H$  for heat transfer.

- $N_u = 0.6 R_e^{0.5} (R_e \leq 2 \times 10^4), N_u = 0.032 R_e^{0.8} (R_e > 2 \times 10^4)$

Nusselt number for a thin disc (diameter  $d$ ) in air, assuming forced convection.

- $G(f) = \left(\frac{A_o}{A_s}\right)^2 = \frac{1}{1 + (f/f_0)^2}$

“Power gain” (ie. ratio of square of output amplitude  $A_o$  to square of input amplitude  $A_s$ ) of an RC lowpass filter having half-power frequency  $f_0 = \frac{1}{2\pi RC}$ .

---

<sup>3</sup>Symbols  $\kappa, D_H$  are both used for this quantity.