

Which receiver would you choose to measure the voltage drop across R_1 ? Why?

